

Lab 0: Comparator Quartus II

Brandon Chin

CSC343 - Instructor: Prof. Izidor Gertner

2/27/2015

Objective:

In Lab 0, we designed an 8-Bit Comparator in ModelSim. Now we must modify the lab to work in Quartus II. Then we must assign pins in order to display the functionality of our design on a DE2 Circuit Board.

Functionality an Specifications

1-Bit Comparator

First, a 1-bit comparator is created. This takes in two inputs, I0 and I1, and returns one output, Eq. The 1-bit comparator will now compare these two inputs, and check for equality. The return value, Eq, will be 0 if the inputs are not equal to each other, or 1 if they are equal to each other.

1-bit comparator VHDL file:

```
1  Library ieee;
2  Use ieee.std_logic_1164.all;
3
4  Entity equal is
5  Port (
6    I0, I1  : in std_logic;
7    Eq  : out std_logic);
8  End equal;
9
10 Architecture arch of equal is
11   Signal P0, P1 : std_logic;
12   begin
13     Eq <= P0 or P1;
14     P0 <= (not I0) and (not I1);
15     P1 <= I0 and I1;
16   End arch;
```

8-Bit Comparator

Now, we will use port mapping to connect eight 1-bit comparators together in order to create the 8-bit comparator. Our inputs are "a" and "b", where these are each 8 bits long, and our output is "aeqb", which is also 8 bits long.

8-bit comparator VHDL file:

```


1  Library ieee;
2  Use ieee.std_logic_1164.all;
3
4  Entity eight_bit_equal_port is
5  Port (
6    a, b: in std_logic_vector(7 downto 0);
7    aeqb : out std_logic);
8  End eight_bit_equal_port;
9
10 Architecture arch of eight_bit_equal_port is
11
12  -- component declaration...we are telling the compiler which
13  -- components we want to use from the library.
14  Component equal
15  Port (
16    I0, I1: in std_logic;
17    Eq : out std_logic);
18  End component;
19
20  signal e0,e1,e2,e3,e4,e5,e6,e7: std_logic;
21  begin
22    --instantiates eight one-bit comparators
23    H1: equal
24    port map(i0=>a(0), i1=>b(0), eq=>e0);
25    H2: equal
26    port map(i0=>a(1), i1=>b(1), eq=>e1);
27    H3: equal
28    port map(i0=>a(2), i1=>b(2), eq=>e2);
29    H4: equal
30    port map(i0=>a(3), i1=>b(3), eq=>e3);
31    H5: equal
32    port map(i0=>a(4), i1=>b(4), eq=>e4);
33    H6: equal
34    port map(i0=>a(5), i1=>b(5), eq=>e5);
35    H7: equal
36    port map(i0=>a(6), i1=>b(6), eq=>e6);
37    H8: equal
38    port map(i0=>a(7), i1=>b(7), eq=>e7);
39    -- a and b are equal if individual bits are equal.
40    aeqb <= e0 and e1 and e2 and e3 and e4 and e5 and e6 and e7;
41  end arch;

```

Simulation

Vector Waveform Simulation:

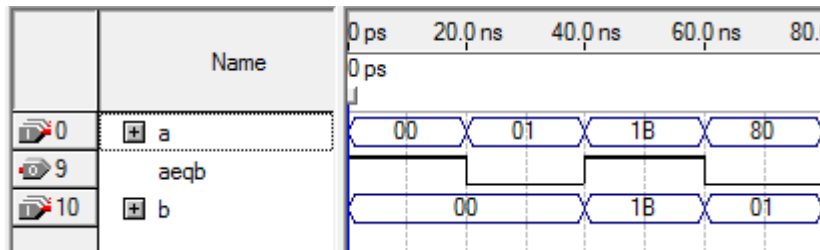In order to test the 8-bit comparator, we will create a vector waveform file (.vwf) for the comparator. Then we will run this simulation, and verify the results.



Here, we can see that our results are indeed correct. Looking at the simulation, the following cases were tested (values are represented in hexadecimal notation):

Case 1: $a = 00$

$b = 00$

$aeqb = 1$

Case 2: $a = 01$

$b = 00$

$aeqb = 0$

Case 3: $a = 1B$

$b = 1B$

$aeqb = 1$

Case 4: $a = 80$

$b = 01$

$aeqb = 0$

DE2 Board Test:


Before connecting to the DE2 board, we will first assign the correct pins to each component of the circuit. The inputs will be assigned to the board's toggle switches, and the output will be assigned to the first red LED light.


Pin assignments text file:

```
1  to, location
2
3  a[0], PIN_N25
4  a[1], PIN_N26
5  a[2], PIN_P25
6  a[3], PIN_AE14
7  a[4], PIN_AF14
8  a[5], PIN_AD13
9  a[6], PIN_AC13
10 a[7], PIN_C13
11
12 b[0], PIN_B13
13 b[1], PIN_A13
14 b[2], PIN_N1
15 b[3], PIN_P1
16 b[4], PIN_P2
17 b[5], PIN_T7
18 b[6], PIN_U3
19 b[7], PIN_U4
20
21 aeqb, PIN_AE23
```

Now we can start the simulation. The first test will check two equal inputs and verify that the LED output light turns on, indicating "aeqb" returns true. Then we will check a case where the inputs are not equal, thus resulting in the LED output light turning off.

Test 1:

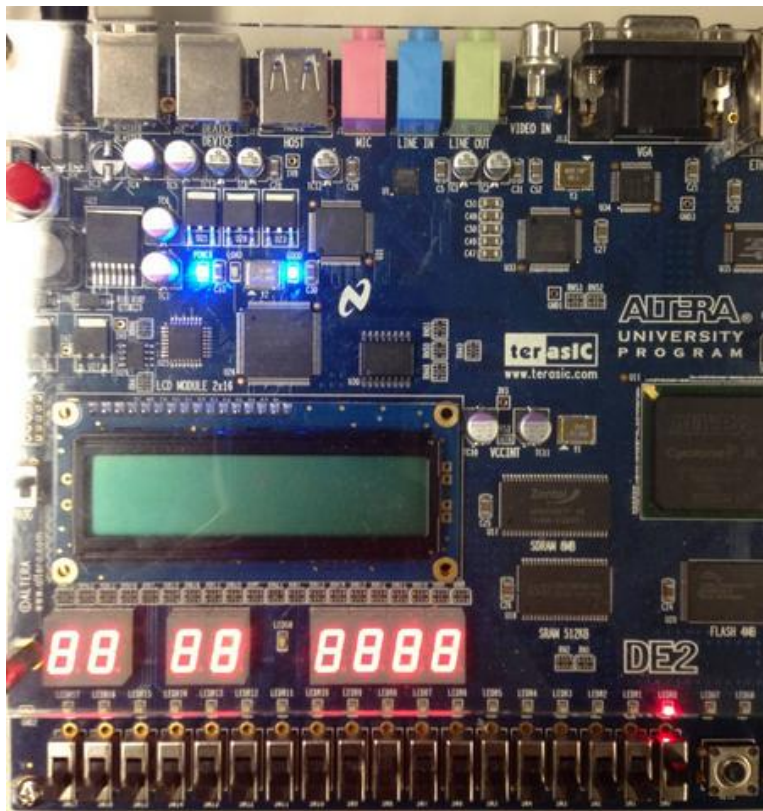

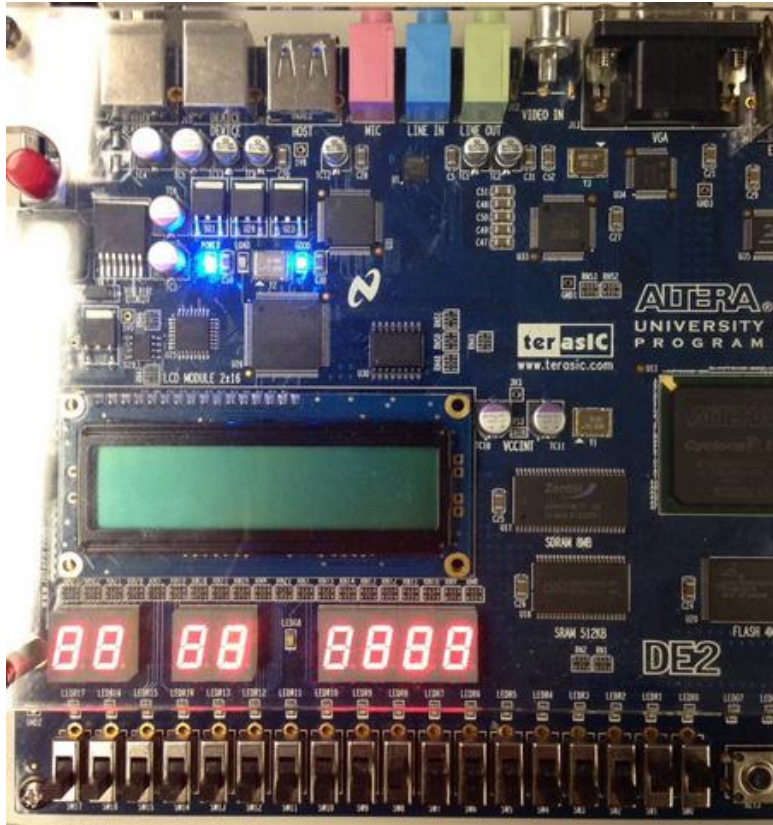Test 2:**Conclusion:**

We began by importing our 1-bit comparator from the previous lab. Then we imported the 8-bit comparator which is built off port mapping eight 1-bit comparators in sequence. We learned how to run vector waveform simulations in Quartus II. We also learned how to test our circuit designs on a DE2 board, which serves as an extension to our Quartus II project. This can become very useful, and we intend to continue using Quartus II and the DE2 board for future labs.